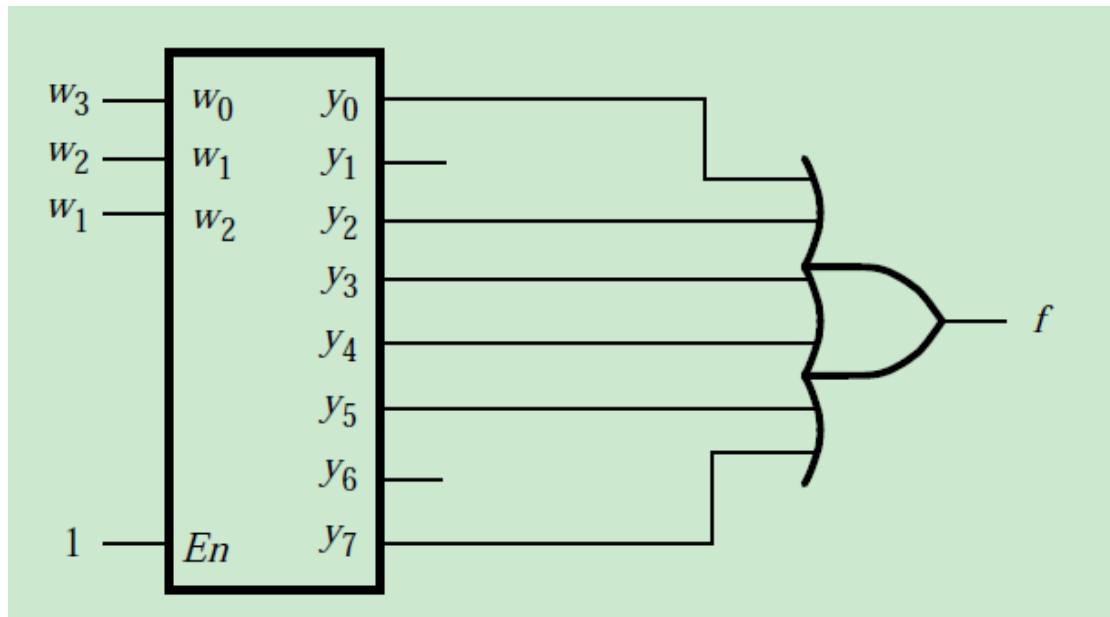


4.1



4.5


The function  $f$  can be expressed as

$$f = \bar{w}_1 \bar{w}_2 \bar{w}_3 + \bar{w}_1 w_2 \bar{w}_3 + \bar{w}_1 w_2 w_3 + w_1 w_2 \bar{w}_3$$

Expansion in terms of  $w_1$  produces

$$f = \bar{w}_1(w_2 + \bar{w}_3) + w_1(w_2 \bar{w}_3)$$


The corresponding circuit is

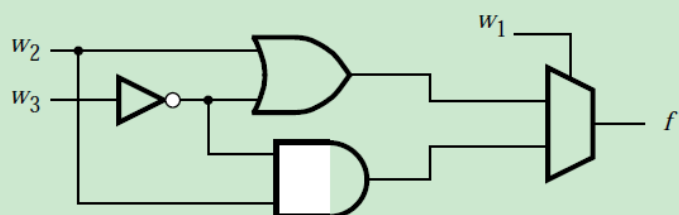


4.19

```
module prob4_19 (W, f);  
  input [1:3] W;  
  output reg f;  
  
  always @(W)  
    case (W)  
      3'b001: f = 1;  
      3'b010: f = 1;  
      3'b011: f = 1;  
      3'b101: f = 1;  
      3'b110: f = 1;  
      default: f = 0;  
    endcase  
  
endmodule
```

5.4

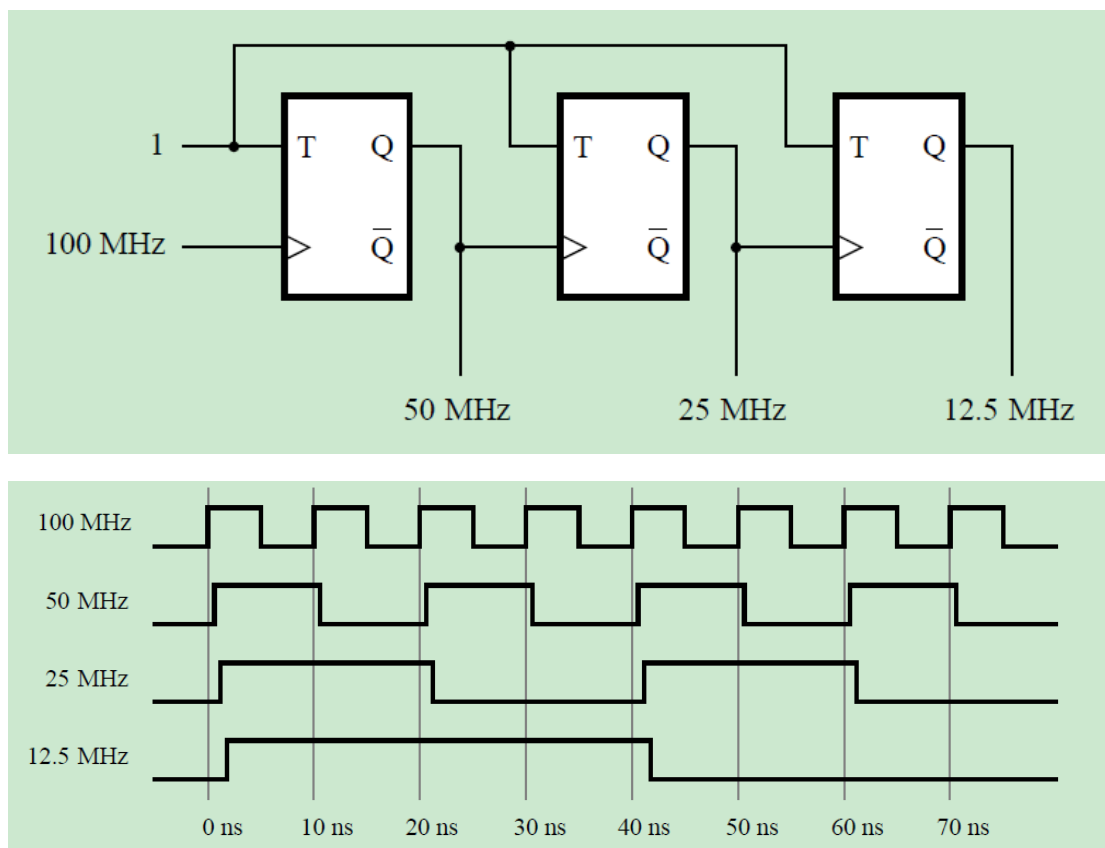

5.7

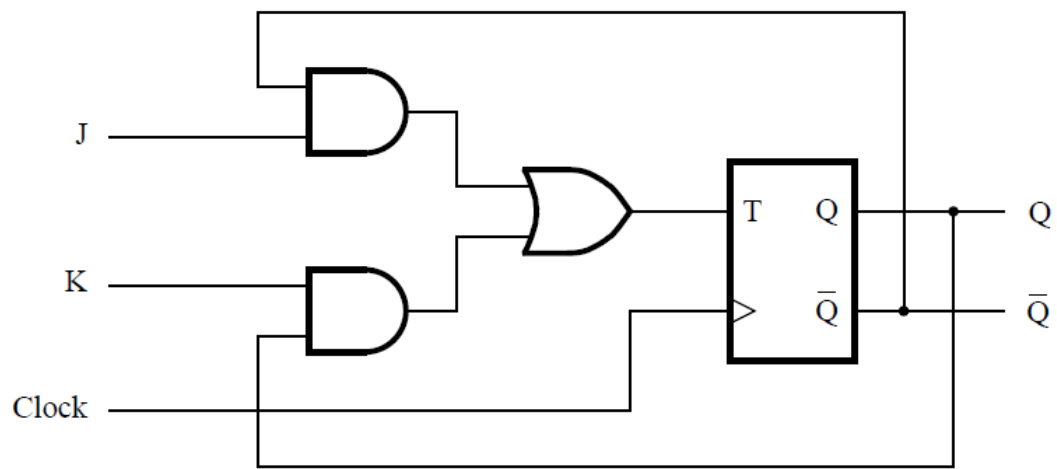

5.13

```
// Universal shift register. If Dir = 0 shifting is to the left.
module universaln (R, L, Dir, w0, w1, Clock, Q);
  parameter n = 4;
  input [n-1:0] R;
  input L, Dir, w0, w1, Clock;
  output reg [n-1:0] Q;
  integer k;


  always @(posedge Clock)
    if (L)
      Q <= R;
    else
      begin
        if (Dir)
          begin
            for (k = 0; k < n-1; k = k+1)
              Q[k] <= Q[k+1];
            Q[n-1] <= w0;
          end
        else
          begin
            Q[0] <= w1;
            for (k = n-1; k > 0; k = k-1)
              Q[k] <= Q[k-1];
          end
        end
      end

endmodule
```

5.24

(a) Period =  $2 \times n \times t_p$

(b)

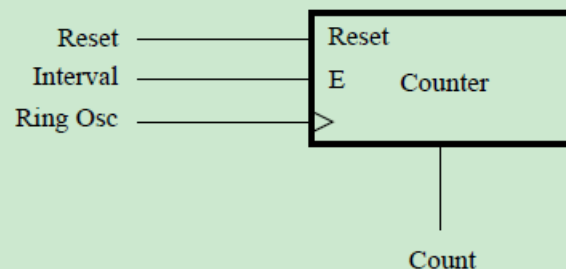

The counter tallies the number of pulses in the 100 ns time period. Thus

$$t_p = \frac{100 \text{ ns}}{2 \times \text{Count} \times n}$$