
 


Chapter 5


5.1.

 


5.2.




5.3.

 


5.4.

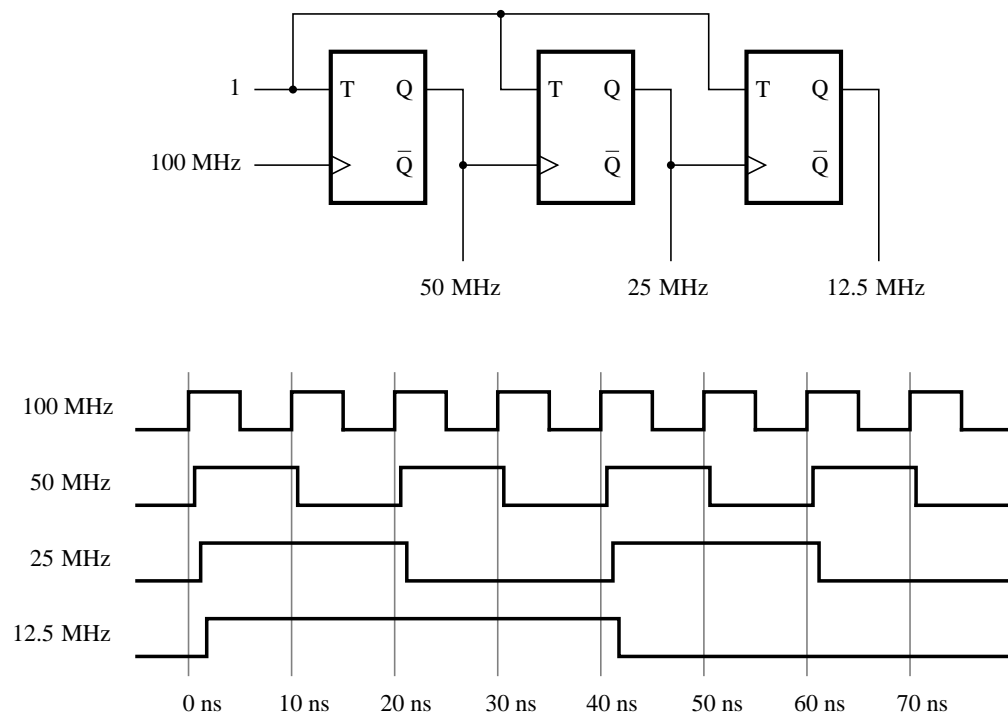

5.5.

 

S	R	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	0

 

[illegible]

The diagram shows a circuit for a JK flip-flop implemented using a D flip-flop and logic gates. The inputs are J, K, and Clock. The outputs are Q and \bar{Q} . The circuit consists of two 2-input AND gates, a 2-input OR gate, and a D flip-flop. The J input is connected to the top input of the first AND gate. The K input is connected to the top input of the second AND gate. The Clock input is connected to the clock input of the D flip-flop and to the bottom inputs of both AND gates. The outputs of the two AND gates are connected to the inputs of the OR gate. The output of the OR gate is connected to the T input of the D flip-flop. The Q output of the D flip-flop is connected to the Q output of the JK flip-flop. The \bar{Q} output of the D flip-flop is connected to the \bar{Q} output of the JK flip-flop. There is also a feedback loop from the Q output of the JK flip-flop to the J input of the first AND gate, and from the \bar{Q} output of the JK flip-flop to the K input of the second AND gate.

```

graph LR
    A((A)) --- NOT1[NOT]
    A --- AND1_1[AND]
    B((B)) --- AND1_2[AND]
    NOT1 --- AND1_1
    AND1_1 --- OR1_1[OR]
    C((C)) --- AND2_1[AND]
    C --- AND2_2[AND]
    C --- OR1_2[OR]
    C --- AND3_1[AND]
    C --- AND3_2[AND]
    AND2_1 --- OR1_1
    AND2_2 --- OR1_2
    AND3_1 --- OR2_1[OR]
    AND3_2 --- OR2_2[OR]
    OR1_1 --- D((D))
    OR2_1 --- E((E))
    OR2_2 --- E
  
```

5-3


5.9.

```
module tflipflop (T, Clock, Resetn, Q);  
  input T, Clock, Resetn;  
  output reg Q;  
  
  always @(negedge Resetn, posedge Clock)  
    if (!Resetn)  
      Q <= 0;  
    else if (T)  
      Q <= Q;  
  
endmodule
```

5.10.

```
module jkflipflop (J, K, Clock, Resetn, Q);  
  input J, K, Clock, Resetn;  
  output reg Q;  
  
  always @(negedge Resetn, posedge Clock)  
    if (!Resetn)  
      Q <= 0;  
    else  
      case (J, K)  
        1'b01:  Q <= 0;  
        1'b10:  Q <= 1;  
        1'b11:  Q <= Q;  
        default: Q <= Q;  
      endcase  
  
endmodule
```

5.12. A possible circuit is

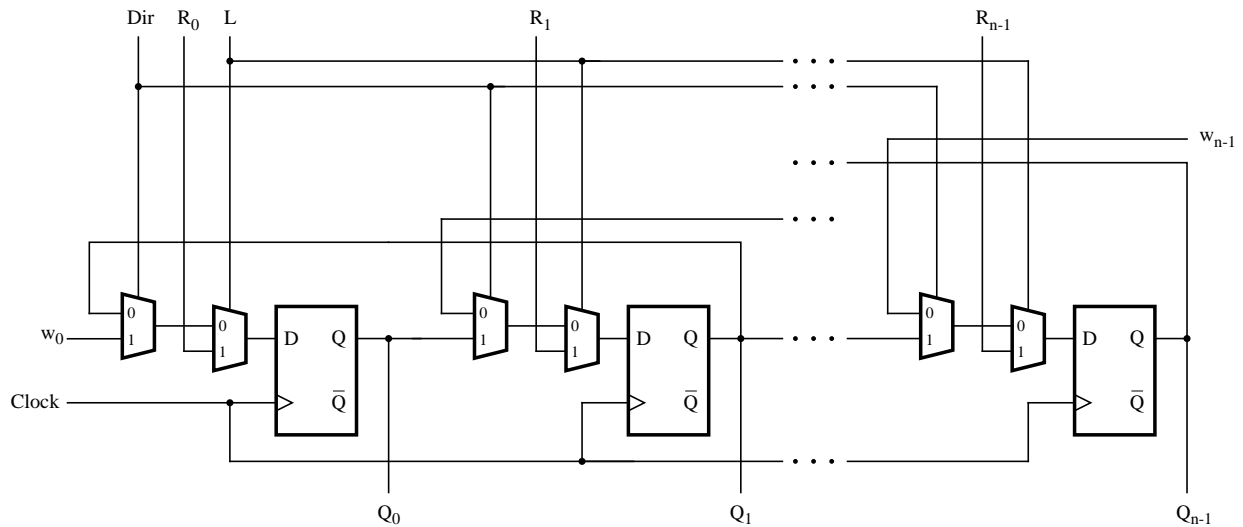

5.13.

// Universal shift register. If Dir = 0 shifting is to the left.

module universaln (R, L, Dir, w0, w1, Clock, Q);

parameter n = 4;

input [n-1:0] R;

input L, Dir, w0, w1, Clock;

output reg [n-1:0] Q;

integer k;

always @(posedge Clock)

if (L)

 Q <= R;

else

begin

if (Dir)

begin

for (k = 0; k < n-1; k = k+1)

 Q[k] <= Q[k+1];

 Q[n-1] <= w0;

end

else

begin

 Q[0] <= w1;

for (k = n-1; k > 0; k = k-1)


 Q[k] <= Q[k-1];

end


end

endmodule


5.14.

 

5.15.

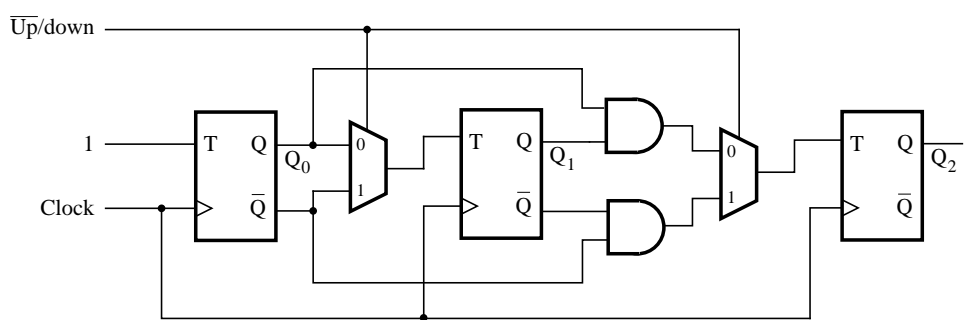


5.16.

 

5.17. The counting sequence is 000, 001, 010, 111.

5.18. The circuit in Figure P5.4 is a master-slave JK flip-flop. It suffers from a problem sometimes called *ones-catching*. Consider the situation where the Q output is low, $Clock = 0$, and $J = K = 0$. Now let $Clock$ remain stable at 0 while J change from 0 to 1 and then back to 0. The master stage is now set to 1 and this value will be incorrectly transferred into the slave stage when the clock changes to 1.

 5.19. Repeated application of DeMorgan's theorem can be used to change the positive-edge triggered D flip-flop in Figure 5.11 into the negative-edge D triggered flip-flop:



5.20.

```
module upcount12 (Resetn, Clock, Q);
  input Resetn, Clock;
  output reg [3:0] Q;

  always @(posedge Clock)
    if (!Resetn)
      Q <= 0;
    else if (Q == 11)
      Q <= 0;
    else
      Q <= Q + 1;

endmodule
```

5.21. The longest delay in the circuit is the from the output of FF_0 to the input of FF_3 . This delay totals 5 ns. Thus the minimum period for which the circuit will operate reliably is

$$T_{min} = 5 \text{ ns} + t_{su} = 8 \text{ ns}$$

The maximum frequency is

$$F_{max} = 1/T_{min} = 125 \text{ MHz}$$

5.22.

```
module johnson8 (Resetn, Clock, Q);
  input Resetn, Clock;
  output reg [7:0] Q;
  reg [7:0] Q;

  always @(negedge Resetn, posedge Clock)
    if (!Resetn)
      Q <= 0;
    else
      Q <= {{Q[6:0]}, {~Q[7]}};

endmodule
```


5.23.


```
// Ring counter with synchronous reset
module ripplen (Resetn, Clock, Q);
  parameter n = 8;
  input Resetn, Clock;
  output reg [n-1:0] Q;

  always @(posedge Clock)
    if (!Resetn)
      begin
        Q[7:1] <= 0;
        Q[0] <= 1;
      end
    else
      Q <= {{Q[6:0]}, {Q[7]}};

endmodule
```

5.24. (a) $\text{Period} = 2 \times n \times t_p$



(b)

 


The counter tallies the number of pulses in the 100 ns time period. Thus

$$t_p = \frac{100 \text{ ns}}{2 \times \text{Count} \times n}$$

5.25.

  


5.26.

 


5.27. With non-blocking assignments, the result of the assignment $f \leftarrow A[1] \& A[0]$ is not seen by the successive assignments inside the **for** loop. Thus, f has an uninitialized value when the **for** loop is entered. Similarly, each **for** loop iteration sees the uninitialized value of f . The result of the code is the sequential circuit specified by $f = f \mid A[n-1] A[n-2]$.

5.28.

 


The counting sequence is: 001, 110, 011, 111, 101, 100, 010, 001

5.29.

 


The counting sequence is: 001, 101, 111, 110, 011, 100, 010, 001

5.30.

 

The counting sequence is: 001, 100, 000, 000, ...

5.31.

 

The counting sequence is: 001, 110, 000, 000, ...

5.32. The required shift register is the same as the one in Figure 5.59, except that the order of the two multiplexers that feed each flip-flop is reversed. The circuit structure is indicated in the figure below.

